

Working Principle of Digital Logic

Model Exam Question paper - 1

11th Standard

Computer Science

Reg.No. :

--	--	--	--	--	--

I. Answer all the questions.

II. Use blue pen only.

Time : 01:00:00 Hrs

Total Marks : 40

10 x 1 = 10

Part-A

- 1) Which is an elementary building block of the digital circuit?
(a) Gate (b) Digital gate (c) Logic gate (d) Physical gate
- 2) The fundamental logic gates are.....
(a) five (b) four (c) two (d) three
- 3) How many possible inputs to AND gate?
(a) 5 (b) 2 (c) 3 (d) 4
- 4) Which one of the following gate is called logical inverter?
(a) NAND (b) XOR (c) NOR (d) NOT
- 5) NOR gate can be replaced by.....
(a) OR (b) AND (c) NAND (d) Bubbled AND
- 6) The output of XOR gate is.....
(a) $C = \bar{A}.B + A.\bar{B}$ (b) $C = \bar{A}.\bar{B} + A.B$ (c) $C = \bar{A}.B + A.B$ (d) $C = \bar{A} + B + \bar{A}.B$
- 7) The output of XNOR is.....
(a) $C = A \otimes B$ (b) $C = \bar{A} \oplus \bar{B}$ (c) $C = \bar{A} \oplus B$ (d) $C = \bar{A} \odot \bar{B}$
- 8) Which can be used to implement the fundamental logic gates?
(a) XOR (b) NAND+NOR (c) XNOR (d) Bubbled AND gate
- 9) To use logic converter, an individual circuit is limited to.....inputs and.....output.
(a) 8,0 (b) 8,1 (c) 7,0 (d) 7,1
- 10) A simplest way to convert a truth table to a Boolean function is.....
(a) NOR of minterms (b) OR minterms (c) OR of maxterms (d) XOR of minterms

Part-B

10 x 2 = 20

- 11) What is a logic gate?
- 12) List the fundamental logical gates.
- 13) Why are NAND and NOR gates called universal gates?
- 14) How can AND gate be realized using NOR gate?
- 15) Give the truth table of XOR gates for two inputs.
- 16) What is synchronous sequential circuit?
- 17) What is electronic workbench?
- 18) What is a logic converter?What purpose does it serve?
- 19) Write the symbol of AND gate and OR gate.
- 20) Define OR gate

Part-C

2 x 5 = 10

- 21) Realize the Boolean function to a logic circuit: $E = \bar{A}B + \bar{B}C + ABC$
- 22) How will you convert the Boolean $D = (A.B) + \bar{C}$ function into a truth table?
